

# MIPS

1. Υλοποίηση και έλεγχος μονάδων.....	1
1.1.1 ALU.....	1
1.1.2 Register file.....	2
1.1.3. data memory.....	2
1.1.4. Instruction memory.....	2
1.1.5. Control.....	2
1.1.6. Control ALU.....	2
1.1.7. Program counter.....	2
1.1.8. 5mux 2-1.....	2
1.1.9. Sign Extention.....	2
1.1.10. 32mux 2-1.....	2
1.1.11. Left Shift.....	2
1.1.12. Adder 32bit.....	2
2 .Υλοποίηση και έλεγχος του επεξεργαστή.....	2
2.1 Entity MIPS.....	2
2.2 Εντολές.....	2
2.3 Ανάπτυξη architecture του MIPS.....	2
2.4 Προσομοίωση - Έλεγχος λειτουργιών.....	2
2.4.1 Ρύθμιση ρολογιού.....	2
2.4.2 Reset.....	2
2.4.3 Προσομοίωση.....	2
2.3.4 ΑΠΟΤΕΛΕΣΜΑΤΑ :.....	2

# 1. Υλοποίηση και έλεγχος μονάδων

## 1.1.1 ALU

**Main :**

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  ENTITY alu IS
6  port (
7      in1      : in  std_logic_vector(31 downto 0);
8      in2      : in  std_logic_vector(31 downto 0);
9      op       : in  std_logic_vector(3 downto 0);
10     outALU    : out std_logic_vector(31 downto 0);
11     Zero      : out std_logic);
12 END alu;
13
14 ARCHITECTURE ALU_1 of ALU is
15     component FullAddder
16     port (
17         in1, in2 : in  std_logic_vector(31 downto 0);
18         carryin  : in  std_logic_vector(0 downto 0);
19         sum      : out std_logic_vector(31 downto 0);
20         carryout : out std_ulogic);
21     end component;
22     component Shifter
23     port (
24         Sin : in  std_logic_vector(31 downto 0);
25         Sout : out std_logic_vector(31 downto 0);
26         opS  : in  std_ulogic;
27         num  : in  std_logic_vector(4 downto 0));
28     end component;
29     signal op_shifter: std_logic;
30     signal carryout:   std_logic;
31     signal out_FA:     std_logic_vector(31 downto 0);
32     signal out_SH:     std_logic_vector(31 downto 0);
33     signal x:          std_logic_vector(31 downto 0) := (others=>'X');
34     signal slt_result: std_logic_vector(31 downto 0);
35 BEGIN
36
37     op_shifter <=
38         '0' when op="0111" else
39         '1' when op="1000" else
40         'X';
41
42     FA_ALU: FullAddder port map(in1 => in1, in2 => in2, carryin => "0", sum => out_FA, carryout=>carryout);
43     SH_ALU: Shifter   port map(Sin => in1, Sout => out_SH, opS => op_shifter, num => in2(4 downto 0));
44
45     slt_result <=
46         std_logic_vector(to_unsigned(1,32)) when (to_integer(signed(in1)) < to_integer(signed(in2))) else
47         std_logic_vector(to_unsigned(0,32));
48
49     with op select
50     outALU <=
51         -- sum:
52         out_FA when "0001",

```

```

53      -- and:
54      in1 and in2 when "0010",
55      -- or:
56      in1 or in2 when "0011",
57      -- nor:
58      in1 nor in2 when "0100",
59      -- and immediate:
60      in1 and in2 when "0101",
61      -- or immediate:
62      in1 or in2 when "0110",
63      -- shift left:
64      out_SH when "0111",
65      -- shift right
66      out_SH when "1000",
67      -- slt
68      slt_result when "1100",
69      -- addi
70      out_FA when "1101",
71
72      std_logic_vector(signed(in1) - signed(in2)) when "1010", -- beq comparison
73      std_logic_vector(signed(in1) - signed(in2)) when "1011", -- bne comparison
74      x when others;
75
76      -- Zero = '1' when ALU result is zero (registers are equal)
77      -- Zero = '0' when ALU result is non-zero (registers are not equal)
78      Zero <=
79      '1' when (in1 = in2) else
80      '0';
81
82      END ALU_1;


```

## TestBench

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity ALU_tb is
6  end ALU_tb;
7
8  architecture Behavioral of ALU_tb is
9
10     component ALU
11     port (
12         in1      : in  std_logic_vector(31 downto 0);
13         in2      : in  std_logic_vector(31 downto 0);
14         op       : in  std_logic_vector(3 downto 0);
15         outALU   : out std_logic_vector(31 downto 0);
16         zero     : out std_logic;
17     );
18     end component;
19
20     signal in1, in2, outALU : std_logic_vector(31 downto 0);
21     signal op               : std_logic_vector(3 downto 0);
22     signal zero             : std_logic;
23
24     begin
25
26         uut: ALU
27         port map (
28             in1      => in1,
29             in2      => in2,
30             op       => op,
31             outALU   => outALU,
32             zero     => zero
33         );
34
35         process
36         begin
37             -- 1. add: 7 + (-3) = 4
38             in1 <= std_logic_vector(to_signed(7, 32));
39             in2 <= std_logic_vector(to_signed(-3, 32));
40             op  <= "0001"; -- add
41             wait for 10 ns;
42
43             -- 2. add: 6 + (-6) = 0 (zero flag should be '1' if op=1010)
44             in1 <= std_logic_vector(to_signed(6, 32));
45             in2 <= std_logic_vector(to_signed(-6, 32));
46             op  <= "0001"; -- add
47             wait for 10 ns;
48
49             -- 3. sub: 5 - 8 = -3 ? simulate as 5 + (-8)
50             in1 <= std_logic_vector(to_signed(5, 32));
51             in2 <= std_logic_vector(to_signed(-8, 32));
52             op  <= "0001"; -- add/sub using negative in2
53             wait for 10 ns;
54
55             -- 4. addi: same as add
56             in1 <= std_logic_vector(to_signed(10, 32));
57             in2 <= std_logic_vector(to_signed(2, 32)); -- immediate
58             op  <= "0001"; -- add
59             wait for 10 ns;
60
61             -- 5. lw/sw: base + offset
62             in1 <= std_logic_vector(to_signed(100, 32)); -- base
63             in2 <= std_logic_vector(to_signed(16, 32));  -- offset
64             op  <= "0001"; -- add
65             wait for 10 ns;
66
67             -- 6. bne: test when in1 /= in2
68             in1 <= std_logic_vector(to_signed(5, 32));
69             in2 <= std_logic_vector(to_signed(7, 32));
70             op  <= "1011"; -- bne
71             wait for 10 ns;
72
73             -- 7. bne: test when in1 = in2 (zero = '0')
74             in1 <= std_logic_vector(to_signed(8, 32));
75             in2 <= std_logic_vector(to_signed(8, 32));
76             op  <= "1011"; -- bne
77             wait for 10 ns;
78
79             wait;
80         end process;
81
82     end Behavioral;
83

```

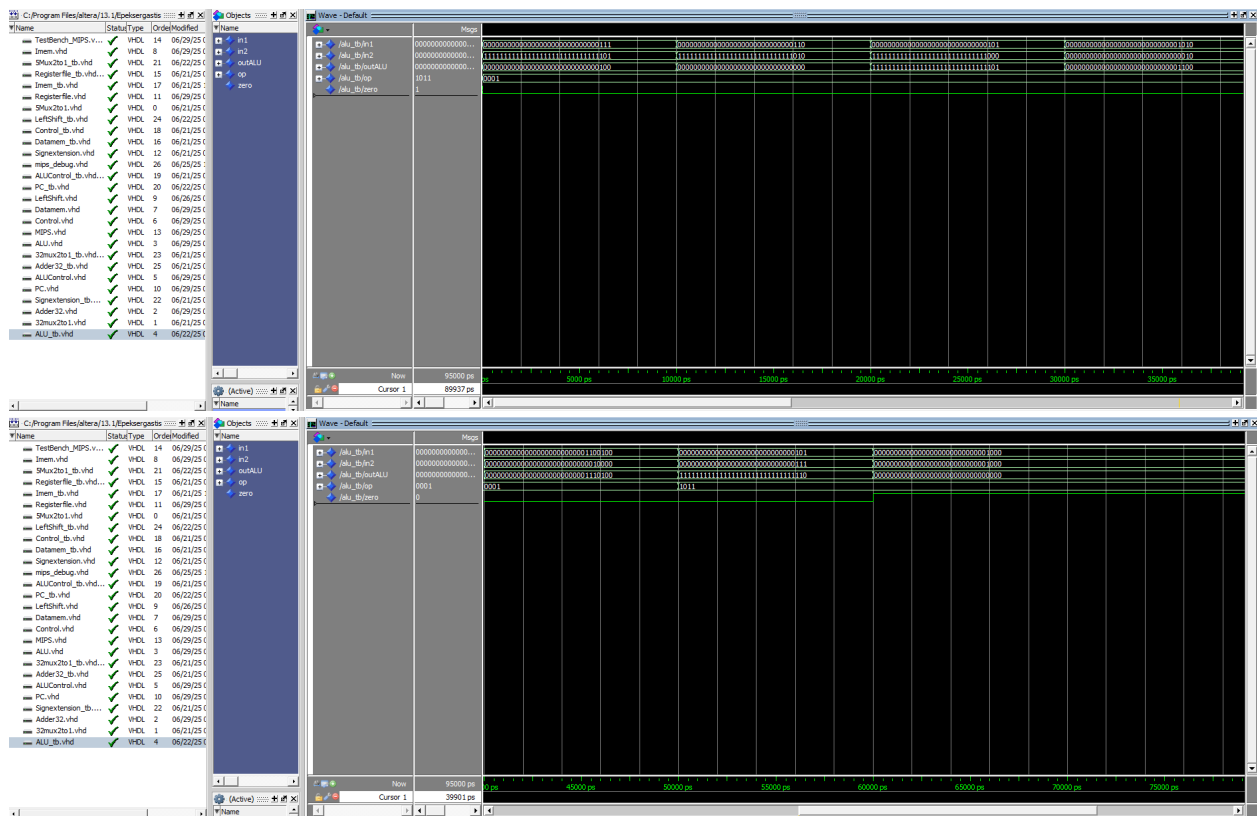

## Σχολια-Παρατηρησεις :

Η alu είναι υπεύθυνη για την εκτέλεση των αριθμητικών και λογικών πράξεων όπως add, sub, and, or, slt, shift, not, addi, επιστρέφει ένα outALU και έχουμε ένα flag για zero που χρησιμοποιείται στην beq και bne

Η alu ενσωματώνει την fulladder, shifter, slt και επιλέγει μια από αυτές με or.

Βλέπουμε ότι πραγματικά για το 1.1.1 της άσκησης, το outALU είναι η σωστή για

$7 + (-3)$ , outALU = 000...100 = 4

$6 + (-6)$ , outALU = 000...000 = 0

$5 - 8$ , outALU = 111..101 = -3

Στο testbench χρησιμοποιώ και άλλες λειτουργικότητες του mips όπως την add, sub, addi, lw, sw, bne

## 1.1.2 Register file

## Main:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  ENTITY Registers is
6  port (
7      CLK          : in  std_logic;
8      RegIn1       : in  std_logic_vector(4 downto 0);
9      RegIn2       : in  std_logic_vector(4 downto 0);
10     RegWriteIn    : in  std_logic_vector(4 downto 0);
11     DataWriteIn   : in  std_logic_vector(31 downto 0);
12     RegWrite      : in  std_logic;
13     RegOut1       : out std_logic_vector(31 downto 0);
14     RegOut2       : out std_logic_vector(31 downto 0);
15 END Registers;
16
17 ARCHITECTURE Registers_1 of Registers is
18     type registers is array (0 to 31) of std_logic_vector(31 downto 0);
19     signal regs: registers := (others=> (others => '0'));
20 BEGIN
21
22     RegOut1 <= regs(to_integer(unsigned(RegIn1))) when to_integer(unsigned(RegIn1)) /= 0 else (others => '0');
23     RegOut2 <= regs(to_integer(unsigned(RegIn2))) when to_integer(unsigned(RegIn2)) /= 0 else (others => '0');
24
25
26     write_process: process(CLK)
27     begin
28         if rising_edge(CLK) then
29             -- Write to register if RegWrite is enabled and not writing to register 0
30             if RegWrite = '1' and to_integer(unsigned(RegWriteIn)) /= 0 then
31                 regs(to_integer(unsigned(RegWriteIn))) <= DataWriteIn;
32             end if;
33         end if;
34     end process;
35
36 END Registers_1;
```

## TestBench :

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity Registerfile_tb is
6  end Registerfile_tb;
7
8  architecture Behavioral of Registerfile_tb is
9
10     component Registers
11     port (
12         clk          : in  std_logic;
13         RegIn1       : in  std_logic_vector(4 downto 0);
14         RegIn2       : in  std_logic_vector(4 downto 0);
15         RegWriteIn   : in  std_logic_vector(4 downto 0);
16         DataWriteIn  : in  std_logic_vector(31 downto 0);
17         RegWrite     : in  std_logic;
18         RegOut1      : out std_logic_vector(31 downto 0);
19         RegOut2      : out std_logic_vector(31 downto 0)
20     );
21     end component;
22
23     -- Signals
24     signal clk          : std_logic := '0';
25     signal RegIn1       : std_logic_vector(4 downto 0);
26     signal RegIn2       : std_logic_vector(4 downto 0);
27     signal RegWriteIn   : std_logic_vector(4 downto 0);
28     signal DataWriteIn  : std_logic_vector(31 downto 0);
29     signal RegWrite     : std_logic;
30     signal RegOut1      : std_logic_vector(31 downto 0);
31     signal RegOut2      : std_logic_vector(31 downto 0);
32
33     constant CLK_PERIOD : time := 10 ns;
34
35 begin
36
37     uut: Registers
38     port map (
39         clk          => clk,
40         RegIn1       => RegIn1,
41         RegIn2       => RegIn2,
42         RegWriteIn   => RegWriteIn,
43         DataWriteIn  => DataWriteIn,
44         RegWrite     => RegWrite,
45         RegOut1      => RegOut1,
46         RegOut2      => RegOut2
47     );
48
49     -- Clock process
50     clk_process : process
51     begin
52         while now < 200 ns loop

```



The screenshot shows the Xilinx Vivado IDE with the Logic Analyzer window open. The window displays a list of signals on the left, a central waveform view, and a bottom status bar. The signals list includes Testbench\_MIPS\_v, Inmem\_vhd, 32mux2to1\_b\_vhd, Registerfile\_b\_vhd, adder1\_vhd, Inmem2\_b\_vhd, Registerfile\_vhd, 32mux2to1\_vhd, Datamem\_b\_vhd, Control\_b\_vhd, Datamem\_b\_vhd, Signextension\_vhd, ALUControl\_b\_vhd, PC\_b\_vhd, LeftShift\_vhd, Datamem\_vhd, Control\_vhd, MIPS\_vhd, ALU\_vhd, 32mux2to1\_b\_vhd, Adder32\_b\_vhd, ALUControl\_vhd, PC\_vhd, Signextension\_b\_vhd, Adder32\_vhd, 32mux2to1\_vhd, and ALU\_b\_vhd. The waveform view shows a time axis from 0 to 40000 ps. The status bar at the bottom indicates the cursor is at 9774 ps.

### Σχολια-Παρατηρησεις :

Σκοπος του register file είναι να αποτελεί ένα πίνακα καταχωρητών του mips και περιλαμβάνει 32 bit καταχωρητές. Κάνω εγγραφή μόνο αν το regwrite = 1 και στην ακμή ρολογιού. Επίσης απαγορεύω την εγγραφή στον \$0 γιατί εκεί η τιμή είναι πάντα 0, αν δωθεί τιμή για τον καταχωρητή αγνοείται.

Test :

Εγγραφή του 6 στον καταχωρητή \$4

Εγγραφή του 9 στον καταχωρητή \$5

Εγγραφή του 3 στον καταχωρητή \$6

Ανάγνωση των καταχωρητών \$4 και \$5

Στην εικόνα βλέπω ότι

RegWritein έχει το \$4 = 0100, \$5 = 00101, \$6 = 00110

DataWritten in έχει 00110 = 6, 1001 = 9, 0011 = 3 και όλα αυτά με regwrite = 1 δηλαδή enabled

Όταν γίνει το regwrite 0 τότε θέλουμε να διαβάσουμε από regin1 = \$4 και regin2 = \$5, και μας δίνει το νούμερο 6 και 9 στο RegOut 1 και RegOut2 αντίστοιχα.

### 1.1.3. data memory

**Main:**

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity Memory is
6      port (
7          CLK          : in  std_logic;
8          inRAM         : in  std_logic_vector(31 downto 0);
9          WriteData     : in  std_logic_vector(31 downto 0);
10         MemWrite      : in  std_logic;
11         MemRead       : in  std_logic;
12         outRAM         : out std_logic_vector(31 downto 0);
13         reset         : in  std_logic
14     );
15 end Memory;
16
17 architecture Memory_1 of Memory is
18     -- RAM: 1024 words of 32-bit memory
19     type ram_type is array (0 to 1023) of std_logic_vector(31 downto 0);
20     signal ram : ram_type := (others => (others => '0'));
21     signal Address : integer := 0;
22
23     -- Function to check if a vector has only defined bits
24     function is_defined(vec : std_logic_vector) return boolean is
25     begin
26         for i in vec'range loop
27             if vec(i) = 'U' or vec(i) = 'X' then
28                 return false;
29             end if;
30         end loop;
31         return true;
32     end function;
33
34 begin
35     -- Address decoding with proper bounds checking
36     process(inRAM)
37         variable temp_addr : integer;
38     begin
39         if is_defined(inRAM) then
40             temp_addr := to_integer(signed(inRAM));
41
42             -- Bounds checking: ensure address is within valid range
43             if temp_addr >= 0 and temp_addr < 1024 then
44                 Address <= temp_addr;
45             else
46                 -- For negative or out-of-bounds addresses, use address 0
47                 Address <= 0;
48             end if;
49         else
50             Address <= 0;
51         end if;
52     end process;
53
54     -- Clocked write to memory
55     process(CLK)
56     begin
57         if rising_edge(CLK) then
58             if (MemWrite = '1' and reset = '0') then
59                 ram(Address) <= WriteData;
60             end if;
61         end if;
62     end process;
63
64     -- Read from memory
65     with reset select
66         outRAM <= ram(Address) when '0',
67                 (others => '0') when others;
68
69 end Memory_1;
70


```

## TestBench

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity Datamem_tb is
6  end Datamem_tb;
7
8  architecture Behavioral of Datamem_tb is
9
10     component Memory
11     port (
12         CLK          : in  std_logic;
13         InRAM        : in  std_logic_vector(31 downto 0);
14         WriteData     : in  std_logic_vector(31 downto 0);
15         MemWrite      : in  std_logic;
16         MemRead       : in  std_logic;
17         outRAM        : out std_logic_vector(31 downto 0);
18         reset         : in  std_logic
19     );
20     end component;
21
22     -- Signals
23     signal CLK          : std_logic := '0';
24     signal InRAM        : std_logic_vector(31 downto 0);
25     signal WriteData    : std_logic_vector(31 downto 0);
26     signal MemWrite     : std_logic := '0';
27     signal MemRead      : std_logic := '0';
28     signal outRAM       : std_logic_vector(31 downto 0);
29     signal reset        : std_logic := '0';
30
31 begin
32
33     -- Instantiate the Unit Under Test (UUT)
34     uut: Memory
35     port map (
36         CLK          => CLK,
37         InRAM        => InRAM,
38         WriteData    => WriteData,
39         MemWrite     => MemWrite,
40         MemRead      => MemRead,
41         outRAM       => outRAM,
42         reset        => reset
43     );
44
45     -- Clock process
46     clk_process : process
47     begin
48         while now < 200 ns loop
49             CLK <= '0';
50             wait for 5 ns;
51             CLK <= '1';
52             wait for 5 ns;
53         end loop;
54     end process;
55
56     -- Stimulus process
57     process
58     begin
59         -- Reset low
60         reset <= '0';
61         wait for 10 ns;
62
63         -- Write 9 to memory address 2
64         InRAM <= std_logic_vector(to_unsigned(2, 32));
65         WriteData <= std_logic_vector(to_signed(9, 32));
66         MemWrite <= '1';
67         wait for 10 ns;
68         MemWrite <= '0';
69
70         -- Write 4 to memory address 3
71         InRAM <= std_logic_vector(to_unsigned(3, 32));
72         WriteData <= std_logic_vector(to_signed(4, 32));
73         MemWrite <= '1';
74         wait for 10 ns;
75         MemWrite <= '0';
76
77         -- Read memory address 2
78         InRAM <= std_logic_vector(to_unsigned(2, 32));
79         MemRead <= '1';
80         wait for 10 ns;
81         MemRead <= '0';
82
83         wait;
84     end process;
85
86 end Behavioral;
87
88

```

 

## Σχολια- Παρατηρησεις :

Σκοπος της Data memory ειναι να αποθηκευσει δεδομενα του προγραμματος για προσωρινες τιμες . Γραφει μονο οταν το MemWrite ειναι Enabled δηλαδη = 1

Test :

Εγγραφή του 9 στη θέση μνήμης 2

Εγγραφή του 4 στη θέση μνήμης 3

Ανάγνωση της θέσης μνήμης 2

Στην εικονα βλεπουμε οτι

InRam = 2 (00..10) γραφει το WriteData = 00...1001 (9)

InRam = 4 (00..100) γραφει το WriteData = 00...0011 (3)

Και επειτα το Memread = 1 και διαβαζουμε το InRam = 2 και μας δινει το

OutRam = 00..1001 (9)

## 1.1.4. Instruction memory

**Main :**


```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  ENTITY InstructionMemory IS
6  port (
7      inIM : in  std_logic_vector(31 downto 0);
8      outIM : out std_logic_vector(31 downto 0)
9  );
10 END InstructionMemory;
11
12 ARCHITECTURE InstructionMemory_1 of InstructionMemory IS
13
14     type mem_type is array (natural range <>) of std_logic_vector(31 downto 0);
15     signal mem : mem_type(0 to 255) := (
16         0 => x"20000000", -- addi $0, $0, 0
17         1 => x"20040000", -- addi $4, $0, 0
18         2 => x"20030001", -- addi $3, $0, 1
19         3 => x"20050003", -- addi $5, $0, 3
20         4 => x"AC830000", -- sw $3, 0($4)
21         5 => x"20630001", -- addi $3, $3, 1
22         6 => x"20840001", -- addi $4, $4, 1
23         7 => x"20A5FFFF", -- addi $5, $5, -1
24         8 => x"14A0FFFF", -- bne $5, $0, L1 (-5)
25         others => x"00000000"
26     );
27
28     signal FullInstruction : std_logic_vector(31 downto 0);
29
30 BEGIN
31
32     process(inIM)
33         variable addr : integer;
34     begin
35         addr := to_integer(unsigned(inIM));
36
37         if (addr >= 0 and addr <= 255) then
38             FullInstruction <= mem(addr);
39         else
40             FullInstruction <= x"00000000";
41             assert false
42                 report "Instruction fetch out of bounds: PC = " & integer'image(addr)
43                 severity note;
44             end if;
45         end process;
46
47         outIM <= FullInstruction;
48
49     END InstructionMemory_1;
50
```

**TestBench :**

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity Imem_tb is
6  end Imem_tb;
7
8  architecture Behavioral of Imem_tb is
9
10     component InstructionMemory
11     port (
12         inIM : in  std_logic_vector(31 downto 0);
13         outIM : out std_logic_vector(31 downto 0)
14     );
15     end component;
16
17     signal inIM : std_logic_vector(31 downto 0);
18     signal outIM : std_logic_vector(31 downto 0);
19
20 begin
21
22     uut: InstructionMemory
23     port map (
24         inIM => inIM,
25         outIM => outIM
26     );
27
28     process
29     begin
30
31         wait for 10 ns;
32
33         inIM <= std_logic_vector(to_unsigned(4, 32));
34         wait for 10 ns;
35
36
37         wait;
38     end process;
39
40 end Behavioral;
41

```

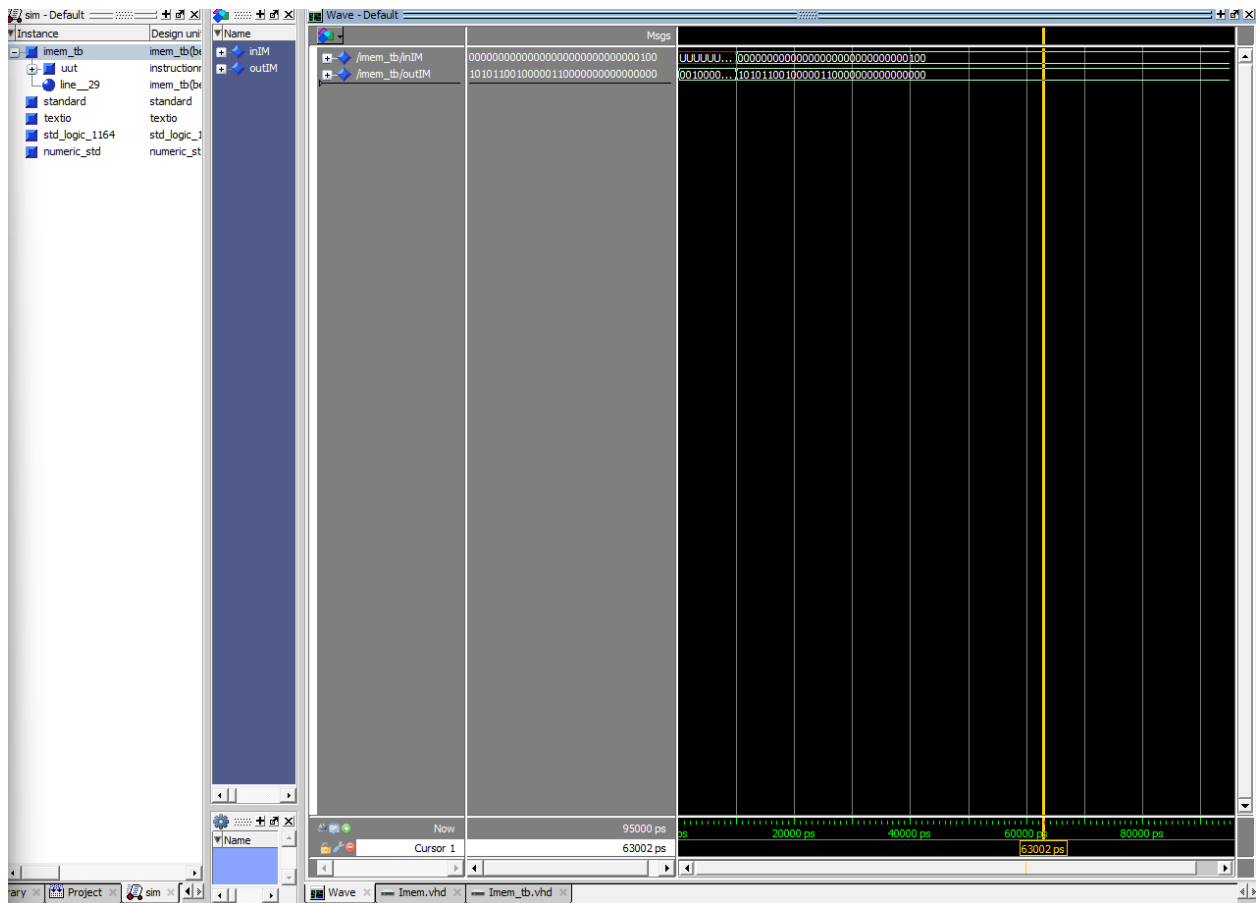

## Σχολια - Παρατηρησεις :

Το instruction memory αποθηκευει τις εντολες που θα εκτελεσει το προγραμμα

Test :

Εγγραφή του Κώδικα 1 στη μνήμη εντολών

(ξεκινώντας από τη θέση 0)

Ανάγνωση της θέσης μνήμης 4.

Στην εικονα βλεπουμε :

Οτι το InIM παει στην διευθυνση 4 ,αυτη που θελουμε να διαβασουμε και επειτα το outim 10101100100000110000000000000000 που ειναι το AC830000 σε δεκαεξαδικο

Εβαλα το report για debugging γιατι στην αρχη ειχα προβληματα με το PC



## 1.1.5. Control

### Main:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  ENTITY OutputControl is
5  port (
6      CLK      : in std_logic;
7      OC_in    : in std_logic_vector(5 downto 0);
8      RegWrite : out std_logic := '0';
9      ALUSrc   : out std_logic;
10     ALUOp     : out std_logic_vector(2 downto 0);
11     MemWrite  : out std_logic;
12     MemRead   : out std_logic;
13     RegDst    : out std_logic;
14     MemToReg  : out std_logic;
15     Jump      : out std_logic;
16     Branch    : out std_logic);
17 END OutputControl;
18
19 ARCHITECTURE OutputControl_1 of OutputControl is
20 BEGIN
21
22     -- Removed the CLK dependency in RegWrite to prevent iteration error loop i was getting
23     with OC_in select
24         RegWrite <=
25             '1' when "100011",--0x23 load by memory
26             '1' when "000000",--0x00 all arithmetic functions
27             '1' when "001000",--0x08 addi
28             '0' when others;
29
30     with OC_in select
31         ALUSrc <=
32             '1' when "100011", --0x23 load word
33             '1' when "101011", --0x2B store word
34             '1' when "001000", --0x08 addi
35             '0' when others;
36
37     with OC_in select
38         ALUOp <=
39             "000" when "000000", --Arith operation
40             "001" when "100011", --RAM operations (load)
41             "001" when "101011", --RAM operations (store)
42             "010" when "000100", --0x04 beq
43             "011" when "000101", --0x05 bne
44             "100" when "001000", --0x08 addi
45             "111" when others;
46
47     with OC_in select
48         MemWrite <=
49             '1' when "101011", --only store
50             '0' when others;
51
52     with OC_in select
53
54         MemRead <=
55             '1' when "100011", --only read
56             '0' when others;
57
58     with OC_in select
59         MemToReg <=
60             '1' when "100011", --only read
61             '0' when others;
62
63     with OC_in select
64         RegDst <=
65             '0' when "100011", --0x23 load word
66             '0' when "001000", --0x08 addi
67             '1' when others;
68
69     with OC_in select
70         Jump <=
71             '1' when "000010", --0x02 jump to address
72             '0' when others;
73
74     with OC_in select
75         Branch <=
76             '1' when "000100", --0x04 beq
77             '1' when "000101", --0x05 bne
78             '0' when others;
79 END OutputControl_1;
```


## TestBench :

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity Control_tb is
5  end Control_tb;
6
7  architecture Control_tb_arch of Control_tb is
8
9      component OutputControl
10         port (
11             CLK          : in  std_logic;
12             OC_in         : in  std_logic_vector(5 downto 0);
13             RegWrite      : out std_logic;
14             ALUSrc        : out std_logic;
15             ALUOp         : out std_logic_vector(2 downto 0);
16             MemWrite      : out std_logic;
17             MemRead       : out std_logic;
18             MemToReg      : out std_logic;
19             RegDst        : out std_logic;
20             Jump          : out std_logic;
21             Branch        : out std_logic
22         );
23     end component;
24
25     -- Signal
26     signal CLK_tb          : std_logic := '0';
27     signal OC_in_tb        : std_logic_vector(5 downto 0);
28     signal RegWrite_tb     : std_logic;
29     signal ALUSrc_tb       : std_logic;
30     signal ALUOp_tb        : std_logic_vector(2 downto 0);
31     signal MemWrite_tb     : std_logic;
32     signal MemRead_tb      : std_logic;
33     signal MemToReg_tb     : std_logic;
34     signal RegDst_tb       : std_logic;
35     signal Jump_tb         : std_logic;
36     signal Branch_tb       : std_logic;
37
38     -- Clock period
39     constant CLK_PERIOD : time := 10 ns;
40
41 begin
42
43     uut: OutputControl
44         port map (
45             CLK          => CLK_tb,
46             OC_in         => OC_in_tb,
47             RegWrite      => RegWrite_tb,
48             ALUSrc        => ALUSrc_tb,
49             ALUOp         => ALUOp_tb,
50             MemWrite      => MemWrite_tb,
51             MemRead       => MemRead_tb,
52             MemToReg      => MemToReg_tb,
```

```

52         memiokey => memiokey_tb,
53         RegDst    => RegDst_tb,
54         Jump      => Jump_tb,
55         Branch    => Branch_tb
56     );
57
58     -- Clock process
59     CLK_process: process
60     begin
61         CLK_tb <= '0';
62         wait for CLK_PERIOD/2;
63         CLK_tb <= '1';
64         wait for CLK_PERIOD/2;
65     end process;
66
67
68     stim_proc: process
69     begin
70         -- Wait for initial setup
71         wait for 20 ns;
72
73         -- Test 1: addi $1, $0, 4 (opcode = 001000)
74         OC_in_tb <= "001000";
75         wait for 30 ns;
76
77         -- Test 2: sw $6, 0($4) (opcode = 101011)
78         OC_in_tb <= "101011";
79         wait for 30 ns;
80
81         -- Test 3: bne $5,$0,L1 (opcode = 000101)
82         OC_in_tb <= "000101";
83         wait for 30 ns;
84
85         -- Additional tests for completeness
86         -- Test lw instruction (opcode = 100011)
87         OC_in_tb <= "100011";
88         wait for 30 ns;
89
90         -- Test R-type instruction (opcode = 000000)
91         OC_in_tb <= "000000";
92         wait for 30 ns;
93
94         wait;
95     end process;
96
97 end Control_tb_arch;

```

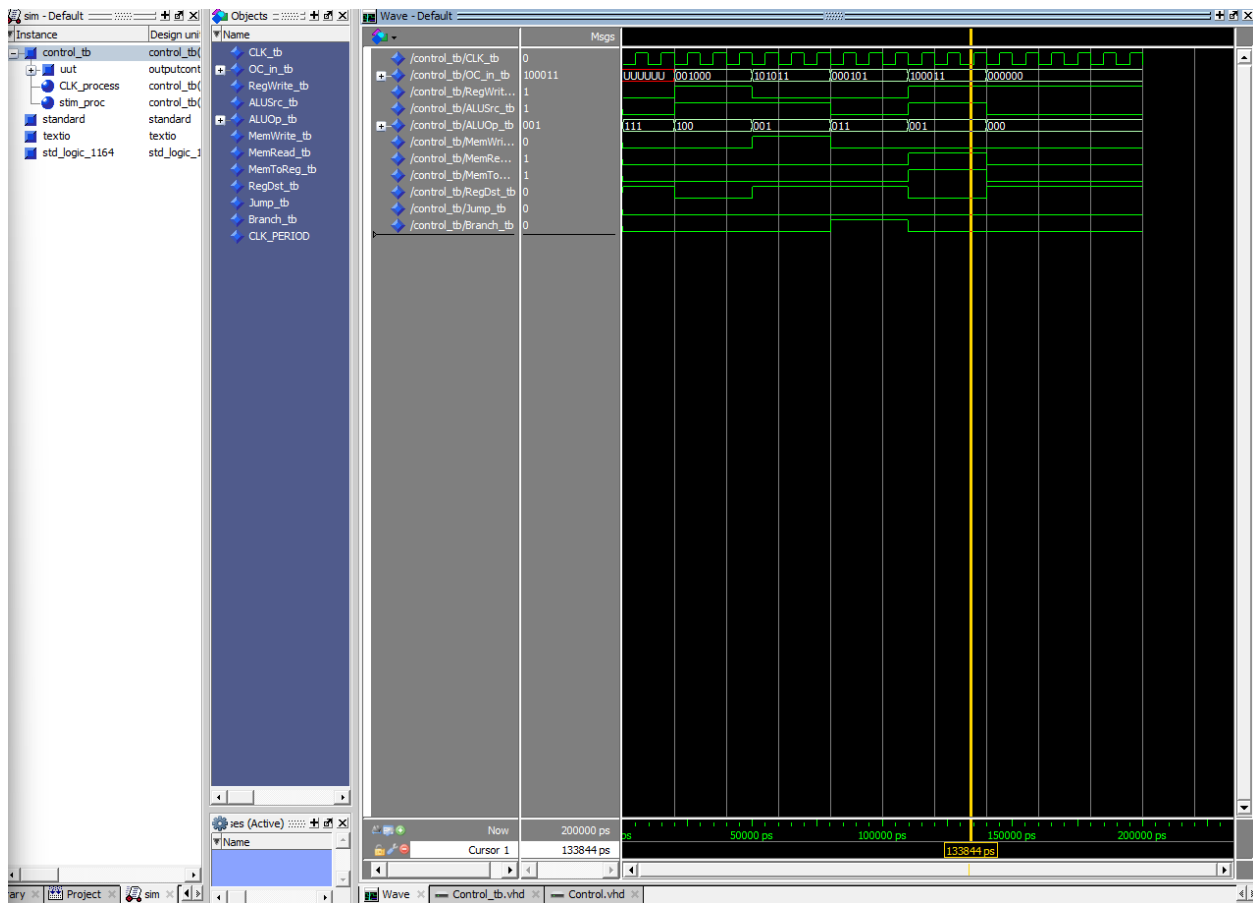

## Σχολια-Παρατηρήσεις :

Το control Unit παίρνει τις εντολές και τις αποκωδικοποιεί και δίνει τα σωστά control signals σε διάφορα μέρη του επεξεργαστή MIPS

Test :

Είσοδος των ακόλουθων εντολών και έλεγχος των εξόδων

addi \$1, \$0, 4

sw \$6, 0(\$4)

bne \$5,\$0,L1

Έχουμε ένα clock ανά 10 ns

1.addi \$1, \$0, 4

Έχουμε

OC\_in = 001000

regwrite = 1 για να γραφει στον register

Alusrc = 1 χρησιμοποιει immediate value , aluop = 111 και regDest = 0

2. sw \$6, 0(\$4)

Oc\_in = 101011

MemWrite = 1 δηλαδή γραφει στην μνημη

Alusrc = 1

AluOP = 001 (ram operations)

3. bne \$5,\$0,L1

Oc\_in = 000101

Branch = 1(γιατι εχουμε branch εντολη)

ALUOP = 011

Επισης εβαλα και

Lw για να δω την λειτουργια και r instruction

Οποτε δινει : oc\_in = 100011

Regwrite = 1 θα γραψει απο μνημη σε register

Memread = 1 αρα θελουμε να διαβασει απο μνημη

Memtoereg = 1 και απο μνημη σε reg

Alusrc = 1

AluOP=001

Επιπλεον : R-Type instruction

Oc\_in = 000000

Regwrite = 1(γραφει αποτελεσμα σε register)

Aluop=000 (arithmetic operation)

Regdst = 1

To simulation δειχνει οτι το control λειτουργει σωστα

## 1.1.6. Control ALU

### Main


```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity ALUControl is port (
5      ALUOp      : in  std_logic_vector(2 downto 0);
6      Funct      : in  std_logic_vector(5 downto 0);
7      ALUCont_out : out std_logic_vector(3 downto 0));
8  end ALUControl;
9
10 architecture ALUControl_1 of ALUControl is
11     signal regALUControl_Funct: std_logic_vector(3 downto 0) :=
12         (others=>'0');
13     signal regALUControl_op: std_logic_vector(3 downto 0) :=
14         (others=>'0');
15
16 begin
17     -- Funct is defined only for R type
18     with Funct select
19         regALUControl_Funct <=
20             "0001" when "100000", --0x20
21             "0010" when "100100", --0x24
22             "0011" when "100101", --0x25
23             "0100" when "100111", --0x27
24             "0101" when "001100", --0x0C
25             "0110" when "001101", --0x0D
26             "0111" when "000000", --0x00
27             "1000" when "000010", --0x02
28             "1100" when "101010", --0x2A slt
29             "1111" when others;
30
31     with ALUOp select
32         regALUControl_op <=
33             "0001" when "001", -- load: add base and relative address
34             "1010" when "010", -- beq
35             "1011" when "011", -- bne
36             "0001" when "100", -- addi
37             "1111" when others;
38
39     with ALUOp select
40         ALUCont_out <=
41             regALUControl_Funct when "000",
42             regALUControl_op when others;
43
44 end ALUControl_1;
```

### TestBench

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity ALUControl_tb is
5  end ALUControl_tb;
6
7  architecture Behavioral of ALUControl_tb is
8
9      component ALUControl
10     port (
11         ALUOp      : in  std_logic_vector(2 downto 0);
12         Funct      : in  std_logic_vector(5 downto 0);
13         ALUCont_out : out std_logic_vector(3 downto 0)
14     );
15     end component;
16
17     signal ALUOp      : std_logic_vector(2 downto 0);
18     signal Funct      : std_logic_vector(5 downto 0);
19     signal ALUCont_out : std_logic_vector(3 downto 0);
20
21     begin
22
23         uut: ALUControl
24         port map (
25             ALUOp      => ALUOp,
26             Funct      => Funct,
27             ALUCont_out => ALUCont_out
28         );
29
30         process
31         begin
32             -- R-type: add => ALUOp = "000", Funct = "100000" (0x20) => ALUCont = "0001"
33             ALUOp <= "000";
34             Funct <= "100000"; -- add
35             wait for 10 ns;
36
37             -- R-type: sub => Funct = "100010"
38             Funct <= "100010";
39             wait for 10 ns;
40
41             -- R-type: and => Funct = "100100" => "0010"
42             Funct <= "100100";
43             wait for 10 ns;
44
45             -- R-type: or => Funct = "100101" => "0011"
46             Funct <= "100101";
47             wait for 10 ns;
48
49             -- R-type: slt => Funct = "101010" => "1100"
50             Funct <= "101010";
51             wait for 10 ns;
52
53             -- I-type: lw/sw => ALUOp = "001" => should output "0001" (add)
54             ALUOp <= "001";
55             wait for 10 ns;
56
57             -- I-type: beq => ALUOp = "010" => "1010"
58             ALUOp <= "010";
59             wait for 10 ns;
60
61             -- I-type: bne => ALUOp = "011" => "1011"
62             ALUOp <= "011";
63             wait for 10 ns;
64
65             -- I-type: addi => ALUOp = "100" => "0001"
66             ALUOp <= "100";
67             wait for 10 ns;
68
69             wait;
70         end process;
71
72     end Behavioral;

```

 

## Σχολια-Παρατηρησεις:

Το ALU control unit λειτουργει με το control unit , παρνει τα signal του και τα μετατρεπει σε συγκεκριμενους κωδικους του για την alu και ετσι η alu κανει την ακριβη πραξη που πρεπει να εκτελεσει .

Τεστ:

Είσοδος των ακόλουθων συνδυασμών και έλεγχος των εξόδων

Funct – ALUOp

100000 – 10

100010 – 10

111111 – 00

111111 – 01

Η funct ειναι μονο για τα r-type instructions

Και για τα i type χρησιμοποιει την aluop

Τι βλεπουμε στο simulation :

1. ALUOp = "000", Funct = "100000" -> ALUCont\_out = "0001" (ADD)



2. ALUOp = "000", Funct = "100010" -> ALUCont\_out = "1111" (SUB)
3. ALUOp = "000", Funct = "100100" -> ALUCont\_out = "0010"(AND)
4. ALUOp = "000", Funct = "100101" -> ALUCont\_out = "0011"(OR)
5. ALUOp = "000", Funct = "101010" -> ALUCont\_out = "1100"(SLT)
6. ALUOp = "001" -> ALUCont\_out = "0001" (LW)
7. ALUOp = "010" -> ALUCont\_out = "1010" (BRANCH EQUAL)
8. ALUOp = "011" -> ALUCont\_out = "1011" (BRANCH NOT EQUAL)
9. ALUOp = "100" -> ALUCont\_out = "0001" (ADDI)

### 1.1.7. Program counter

#### Main


```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  ENTITY ProgramCounter IS
6      port (
7          inPC : in  std_logic_vector(31 downto 0);
8          outPC : out std_logic_vector(31 downto 0);
9          CLK  : in  std_logic;
10         Rst   : in  std_logic
11     );
12 END ProgramCounter;
13
14 ARCHITECTURE ProgramCounter_1 of ProgramCounter IS
15 BEGIN
16     reg: process (CLK,Rst)
17     begin
18         if Rst = '1' then
19             outPC <= (others => '0'); -- clear PC on reset
20         elsif rising_edge(CLK) then
21             outPC <= inPC;           -- update PC on clock edge
22         end if;
23     end process;
24 END ProgramCounter_1;
25
```

#### TestBench

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity PC_tb is
5  end PC_tb;
6
7  architecture PC_tb of PC_tb is
8  -- Component declaration
9  component ProgramCounter
10     port (
11         InPC : in  std_logic_vector(31 downto 0);
12         OutPC : out std_logic_vector(31 downto 0);
13         CLK : in  std_logic;
14         Rst : in  std_logic
15     );
16 end component;
17
18 -- Signal declarations
19 signal InPC_tb : std_logic_vector(31 downto 0);
20 signal OutPC_tb : std_logic_vector(31 downto 0);
21 signal CLK_tb : std_logic := '0';
22 signal Rst_tb : std_logic := '0';
23
24 -- Clock period
25 constant CLK_PERIOD : time := 10 ns;
26
27 begin
28
29     uut: ProgramCounter
30     port map (
31         InPC => InPC_tb,
32         OutPC => OutPC_tb,
33         CLK => CLK_tb,
34         Rst => Rst_tb
35     );
36
37 -- Clock process
38 CLK_process: process
39 begin
40     CLK_tb <= '0';
41     wait for CLK_PERIOD/2;
42     CLK_tb <= '1';
43     wait for CLK_PERIOD/2;
44 end process;
45
46
47 stim_proc: process
48 begin
49
50     wait for 10 ns;
51
52     -- Test reset functionality
53     Rst_tb <= '1';
54     InPC_tb <= x"12345678"; -- Should be ignored during reset
55     wait for 20 ns;
56     Rst_tb <= '0';
57     wait for 10 ns;
58
59     -- Test 1: Write and read 0xAAAACCCC
60     InPC_tb <= x"AAAACCCC";
61     wait for 20 ns; -- Wait for clock edge
62
63     -- Test 2: Write and read 0xFFFFBBBB
64     InPC_tb <= x"FFFFBBBB";
65     wait for 20 ns; -- Wait for clock edge
66
67
68     wait;
69 end process;
70
71 end PC_tb;

```

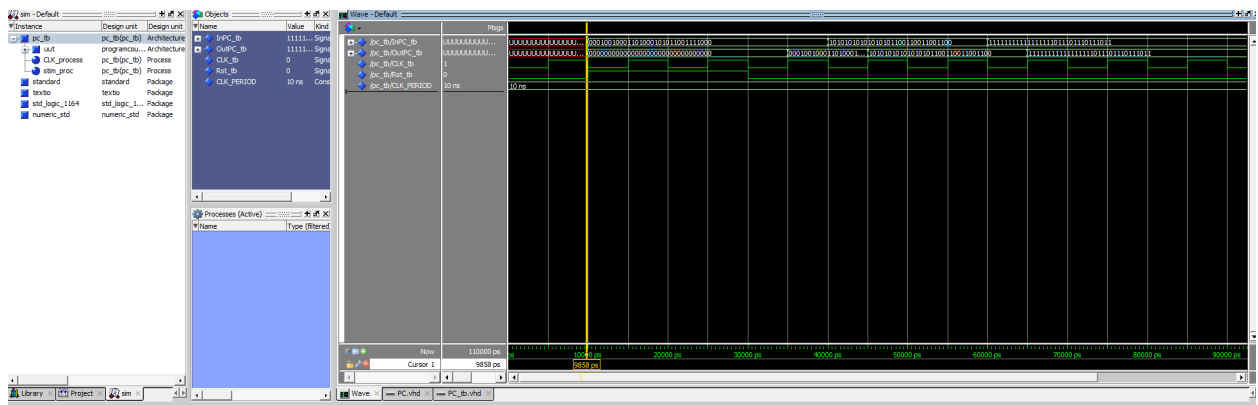

**Σχολια - Παρατηρησεις :**

Ο PC κρατάει τη διεύθυνση της τρέχουσας εντολής

Τεστ:

Εγγραφή και ανάγνωση των ακόλουθων δεδομένων:

0xAAAA CCCC

0xFFFF BBBB

Αρχικά κανουμε ενα reset , Rst= 1 και το outpc δίνει 0 ανεξαρτητως το pcin

Εχω βάλει για τεστ pc in 0x"12345678"

Μετα θετω rst=0 και βαζω το pcin = 0xAAAA CCCC

Το outpc δίνει το περιεχομενο αυτο σε 32 bit

Επειτα βαζω inpc = 0xFFFF BBBB

Outpc = 0xFFFF BBBB.

### 1.1.8. 5mux 2-1

#### **Main**

```

1  Library IEEE;
2  use IEEE.std_logic_1164.all;
3  ENTITY MUX2_5 IS PORT (
4      MUXin1 : in std_logic_vector(4 downto 0);
5      MUXin2 : in std_logic_vector(4 downto 0);
6      MUXout  : out std_logic_vector(4 downto 0);
7      sel    : in std_logic);
8  END MUX2_5;
9  ARCHITECTURE MUX2_5_1 of MUX2_5 is
10 BEGIN
11     MUXout <= MUXin1 when sel='0' else
12             MUXin2 when sel='1';
13 END;
14


```

## TestBench

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity Mux2tol_5_tb is
5  end Mux2tol_5_tb;
6
7  architecture Mux2tol_5_tb of Mux2tol_5_tb is
8      -- Component declaration
9      component MUX2_5
10         port (
11             MUXin1 : in  std_logic_vector(4 downto 0);
12             MUXin2 : in  std_logic_vector(4 downto 0);
13             MUXout  : out std_logic_vector(4 downto 0);
14             sel     : in  std_logic
15         );
16     end component;
17
18     -- Signal declarations
19     signal MUXin1_tb : std_logic_vector(4 downto 0);
20     signal MUXin2_tb : std_logic_vector(4 downto 0);
21     signal MUXout_tb  : std_logic_vector(4 downto 0);
22     signal sel_tb     : std_logic;
23
24 begin
25
26     uut: MUX2_5
27     port map (
28         MUXin1 => MUXin1_tb,
29         MUXin2 => MUXin2_tb,
30         MUXout => MUXout_tb,
31         sel    => sel_tb
32     );
33
34     -- Stimulus process
35     stim_proc: process
36     begin
37         -- Wait for initial setup
38         wait for 10 ns;
39
40         -- E1F0A0E0 - E1F0A0E1 - ENIAOFH
41         -- 0x1C - 0x0A - 1
42         -- 0x1C - 0x0B - 0
43
44         -- Test 1: Input0=0x1C, Input1=0x0A, Select=1 (should output 0x0A)
45         MUXin1_tb <= "11100"; -- 0x1C
46         MUXin2_tb <= "01010"; -- 0x0A
47         sel_tb <= '1';
48         wait for 20 ns;
49
50         -- Test 2: Input0=0x1C, Input1=0x0B, Select=0 (should output 0x1C)
51         MUXin1_tb <= "11100"; -- 0x1C
52         MUXin2_tb <= "01011"; -- 0x0B
53         sel_tb <= '0';
54         wait for 20 ns;
55
56         wait;
57     end process;
58
59 end Mux2tol_5_tb;
60
61
62
63

```

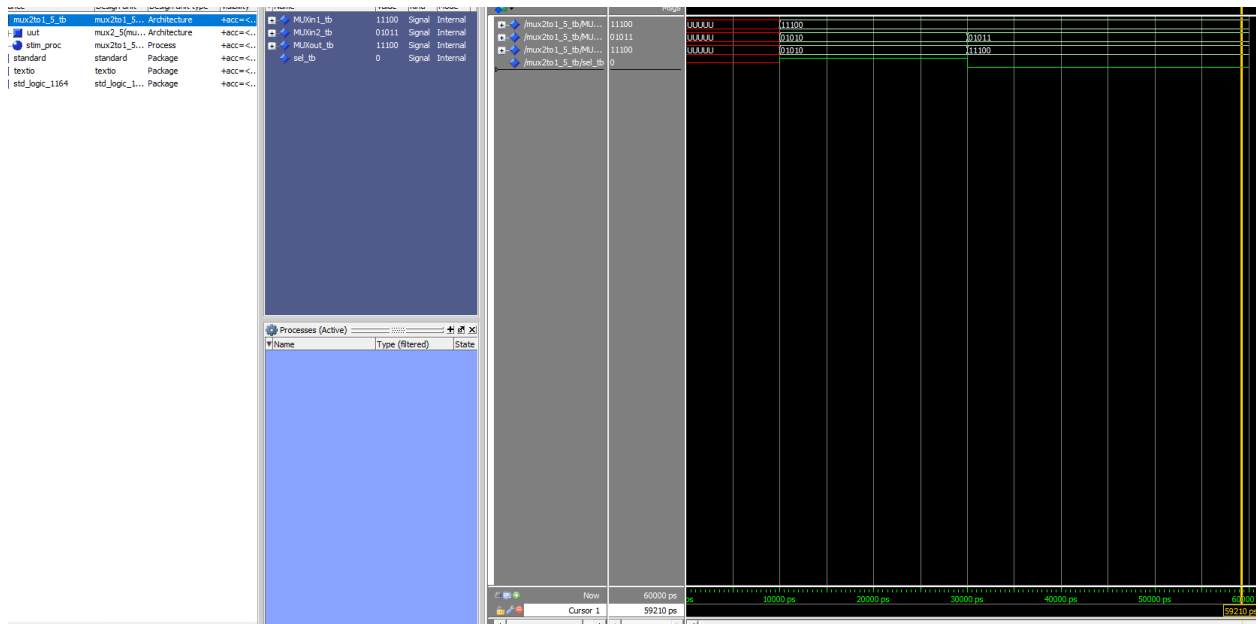

## Σχολια - Παρατηρησεις :

Αυτό είναι ένας 2 to 1 multiplexe **r** που λειτουργεί με 5-bit vectors - χρησιμοποιείται για την επιλογή register destinations στον mips επεξεργαστή.

Τεστ:

ΕΙΣΟΔΟΣ0 – ΕΙΣΟΔΟΣ1 – ΕΠΙΛΟΓΗ

0x1C – 0x0A – 1

0x1C – 0x0B – 0

Όταν sel = 0 τότε muxout = muxin1

Όταν sel = 1 τότε muxout = muxin2

1. 0x1C – 0x0A – 1  
Βλεπουμε muxin1 = 11100 (0x1C)  
Muxin2 = 01010(0x0A)  
Sel = 1  
Muxout = 01010(muxin2)
2. 0x1C – 0x0B – 0  
muxin1 = 11100 (0x1C)  
Muxin2 = 01011(0x0B)

Sel = 0  
Muxout = 11100(muxin1)

### 1.1.9. Sign Extension

#### Main


```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  ENTITY SignExtend IS port (
5      SignExIn  : in  std_logic_vector(15 downto 0);
6      SignExOut : out std_logic_vector(31 downto 0)
7  );
8  END SignExtend;
9
10 ARCHITECTURE SignExtend_1 of SignExtend IS
11     signal ones  : std_logic_vector(15 downto 0) := (others=>'1');
12     signal zeros : std_logic_vector(15 downto 0) := (others=>'0');
13 BEGIN
14
15
16
17     SignExOut <= ones & SignExIn  when SignExIn(15) = '1' else
18                 zeros & SignExIn when SignExIn(15) = '0';
19
20 END SignExtend_1;
```

#### TestBench

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity Signextension_tb is
5  end Signextension_tb;
6
7  architecture Signextension_tb of Signextension_tb is
8      -- Component declaration
9      component SignExtend
10         port (
11             SignExIn  : in  std_logic_vector(15 downto 0);
12             SignExOut : out std_logic_vector(31 downto 0)
13         );
14     end component;
15
16     -- Test signals
17     signal SignExIn_tb  : std_logic_vector(15 downto 0);
18     signal SignExOut_tb : std_logic_vector(31 downto 0);
19
20 begin
21     -- Component instantiation
22     UUT: SignExtend
23         port map (
24             SignExIn  => SignExIn_tb,
25             SignExOut => SignExOut_tb
26         );
27
28     -- Test process
29     stimulus_process: process
30     begin
31         -- Test case 1: 0xFAAA (negative number)
32         SignExIn_tb <= x"FAAA";
33         wait for 10 ns;
34
35         -- Test case 2: 0xFFFF (negative number)
36         SignExIn_tb <= x"FFFF";
37         wait for 10 ns;
38
39         -- Test case 3: 0x5444 (positive number)
40         SignExIn_tb <= x"5444";
41         wait for 10 ns;
42
43         -- End simulation
44         wait;
45     end process;
46
47 end Signextension_tb;
48

```

 

## Σχολια - Παρατηρησεις :

Αυτο το unit παρνει ενα 16 bit signed και το κανει 32 bit signed number

Signexin = 16bit

Signexout = 32 bit

Επισης :

Αν msb (most significant bit)= 1 τότε negative number

Αλλιως positive

Τεστ :

Είσοδος των ακόλουθων συνδυασμών και έλεγχος εξόδων

0xFAAA

0xAFFF

0x5444

Βλεπουμε στο simulation οτι κανανε extend σε

SignOut = 0xFFFFFAAAA (negative number extended)

SignOut = 0xFFFFFAFFF (negative number extended)

SignOut = 0x00005444 (positive number extended)

### 1.1.10. 32mux 2-1


#### Main

```
1
2  Library IEEE;
3  use IEEE.std_logic_1164.all;
4
5  ENTITY MUX2_32 is PORT (
6      MUXin1 : in std_logic_vector(31 downto 0);
7      MUXin2 : in std_logic_vector(31 downto 0);
8      MUXout  : out std_logic_vector(31 downto 0);
9      sel : in std_logic );
10
11  END MUX2_32;
12
13  ARCHITECTURE MUX2_32_1 of MUX2_32 is
14  BEGIN
15      MUXout <= MUXin1 when sel='0' else
16                MUXin2 when sel='1';
17  END MUX2_32_1;
```


 
# TestBench

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity Mux32_2to1_tb is
5  end Mux32_2to1_tb;
6
7  architecture testbench of Mux32_2to1_tb is
8      -- Component declaration
9      component MUX2_32
10         port (
11             MUXin1 : in std_logic_vector(31 downto 0);
12             MUXin2 : in std_logic_vector(31 downto 0);
13             MUXout  : out std_logic_vector(31 downto 0);
14             sel     : in std_logic
15         );
16     end component;
17
18     -- Test signals
19     signal MUXin1_tb : std_logic_vector(31 downto 0);
20     signal MUXin2_tb : std_logic_vector(31 downto 0);
21     signal MUXout_tb : std_logic_vector(31 downto 0);
22     signal sel_tb    : std_logic;
23
24     begin
25         -- Component instantiation
26         UUT: MUX2_32
27             port map (
28                 MUXin1 => MUXin1_tb,
29                 MUXin2 => MUXin2_tb,
30                 MUXout => MUXout_tb,
31                 sel    => sel_tb
32             );
33
34         -- Test process
35         stimulus_process: process
36         begin
37             -- Setup test inputs
38             MUXin1_tb <= x"CCCCCCCC"; -- E1F0A0E0
39             MUXin2_tb <= x"BBBBBBBB";  -- E1F0A0E1
40
41             -- Test case 1: sel = 1 (should select input2)
42             sel_tb <= '1';
43             wait for 10 ns;
44
45             -- Test case 2: sel = 0 (should select input1)
46             sel_tb <= '0';
47             wait for 10 ns;
48
49             -- End simulation
50             wait;
51         end process;
52
53     end testbench;
54
```



## Σχολια - Παρατηρησεις :

Δουλενει σαν τον 5mux 2 to 1 απλα χρησιμοποιει 32 bit inputs

Muxin1 οταν sel = 0

Muxin2 οταν sel =1

Test :

Είσοδος των ακόλουθων συνδυασμών και έλεγχος εξόδων

ΕΙΣΟΔΟΣ0 – ΕΙΣΟΔΟΣ1 – ΕΠΙΛΟΓΗ

0xCCCCCCCC – 0xBBBBBBBB – 1

0xCCCCCCCC – 0xBBBBBBBB – 0

Βλεπουμε :

Για sel = 1

Mux out = muxin2 = 100110... = 0xBBBBBBBB

Για sel = 0

Muxout = muxin1 = 11001.. = 0xCCCCCCCC


### 1.1.11. Left Shift

## Main

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  ENTITY Shifter is
6  port (
7      Sin  : in  std_logic_vector(31 downto 0);
8      Sout : out std_logic_vector(31 downto 0);
9      opS  : in  std_ulogic;
10     num  : in  std_logic_vector(4 downto 0));
11  END Shifter;
12
13  ARCHITECTURE Shifter_1 of Shifter is
14
15     signal tmp: unsigned(31 downto 0);
16
17  BEGIN
18
19     tmp <= to_unsigned(to_integer(signed(Sin)),tmp'length) sll to_integer(signed(num)) when opS='0' else
20     to_unsigned(to_integer(signed(Sin)),tmp'length) srl to_integer(signed(num)) when opS='1';
21
22     Sout <= std_logic_vector(to_signed(to_integer(tmp),Sout'length));
23
24  END Shifter_1;
```
 
## TestBench

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity Leftshift_tb is
6  end Leftshift_tb;
7
8  architecture testbench of Leftshift_tb is
9      -- Component declaration
10     component Shifter
11     port (
12         Sin  : in  std_logic_vector(31 downto 0);
13         Sout : out std_logic_vector(31 downto 0);
14         opS   : in  std_ulogic;
15         num   : in  std_logic_vector(4 downto 0)
16     );
17     end component;
18
19     -- Test signals
20     signal Sin_tb  : std_logic_vector(31 downto 0);
21     signal Sout_tb : std_logic_vector(31 downto 0);
22     signal op_tb   : std_ulogic;
23     signal num_tb  : std_logic_vector(4 downto 0);
24
25     begin
26         -- Component instantiation
27         UUT: Shifter
28         port map (
29             Sin  => Sin_tb,
30             Sout => Sout_tb,
31             opS  => op_tb,
32             num  => num_tb
33         );
34
35         -- Test process
36         stimulus_process: process
37         begin
38             -- Test case: 0xFFFFFFFF left shift by 2 positions
39             Sin_tb <= x"0FFFFFFF";
40             op_tb  <= '0'; -- left shift
41             num_tb <= "00010"; -- shift by 2
42             wait for 10 ns;
43
44             -- Test: shift 0x80000000 right by 1
45             Sin_tb <= x"0FFFFFFF";
46             op_tb  <= '1'; -- right shift
47             num_tb <= "00010";
48             wait for 10 ns;
49
50             wait;
51         end process;
52     end testbench;
53
54 end testbench;
55
```



## Σχολια-Παρατηρησεις:

Το unit αυτο κανει ολισθηση αριστερα κατα 2 σε 32 bit number

Τεστ :

Είσοδος των ακόλουθων συνδυασμών και έλεγχος εξόδων

0x0FFF FFFF

Βλεπουμε οτι

Sin = 0x0FFFFFFF

Op = 0 (left)

Num = 2 (ολισθηση κατα 2)

Αποτελεσμα : 0x3FFFFFFC

Επισης δοκιμασα και right shift

Sin = 0x0FFFFFFF

Op = 1 (right)

Num = 2 (ολισθηση κατα 2)

Αποτελεσμα : 0x03FFFFFF


## 1.1.12. Adder 32bit

### Main

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  ENTITY FullAdder IS port (
6      in1, in2      : in  std_logic_vector(31 downto 0);
7      carryin       : in  std_logic_vector(0 downto 0);
8      sum           : out std_logic_vector(31 downto 0);
9      carryout      : out std_logic);
10 END FullAdder;
11
12 -- Architecture for FullAdder
13 ARCHITECTURE FullAdder_1 of FullAdder is
14     -- Temp signal for sum with 32th for carry
15     signal tmp: std_logic_vector(32 downto 0);
16 BEGIN
17     tmp      <= std_logic_vector(to_signed( to_integer(signed(in1)) + to_integer(signed(in2)) + to_integer(signed(carryin)),33));
18     carryout <= tmp(32);
19     sum      <= tmp(31 downto 0);
20 END FullAdder_1;
21
22
23
24
25
```
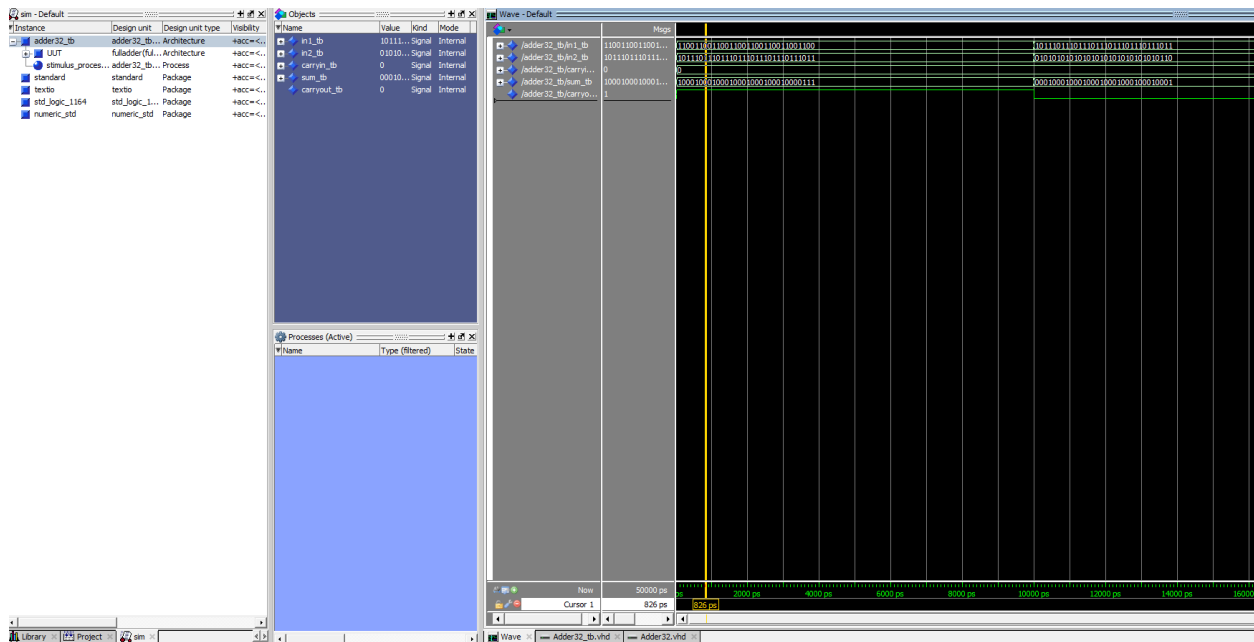
### TestBench

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity Adder32_tb is
6  end Adder32_tb;
7
8  architecture testbench of Adder32_tb is
9      -- Component declaration
10     component FullAdder
11     port (
12         in1, in2      : in  std_logic_vector(31 downto 0);
13         carryin       : in  std_logic_vector(0 downto 0);
14         sum           : out std_logic_vector(31 downto 0);
15         carryout      : out std_logic);
16     );
17     end component;
18
19     -- Test signals
20     signal in1_tb      : std_logic_vector(31 downto 0);
21     signal in2_tb      : std_logic_vector(31 downto 0);
22     signal carryin_tb  : std_logic_vector(0 downto 0);
23     signal sum_tb      : std_logic_vector(31 downto 0);
24     signal carryout_tb : std_logic;
25
26 begin
27     -- Component instantiation
28     UUT: FullAdder
29     port map (
30         in1 => in1_tb,
31         in2 => in2_tb,
32         carryin => carryin_tb,
33         sum => sum_tb,
34         carryout => carryout_tb
35     );
36
37     -- Test process
38     stimulus_process: process
39     begin
40         -- No carry in for both tests
41         carryin_tb <= "0";
42
43         -- Test case 1: 0xCCCCCCCC + 0xBBBBBBBB
44         in1_tb <= x"CCCCCCCC";
45         in2_tb <= x"BBBBBBBB";
46         wait for 10 ns;
47
48         -- Test case 2: 0xBBBBBBBB + 0x55555556
49         in1_tb <= x"BBBBBBBB";
50         in2_tb <= x"55555556";
51         wait for 10 ns;
52
53         -- End simulation
54         wait;
55     end process;
56
57 end testbench;
58
```



## Σχολια - Παρατηρησεις :

Ο adder είναι ένα unit που κάνει προσθεσεις με δυο 32 bit number

Εχουμε in1 , in2 που είναι 32 bit αριθμοι και carryin που είναι 1 carry input

Εχουμε ένα sum για τα αποτελεσματα και ένα carry out αν υπαρξει overflow

Μετατρεπει τις εισοδους σε προσημασμενους ακεραιους αριθμους ,εκτελει προσθεση με προσωρινο αποτελεσμα tmp 32 bit και εξαγει το κρατουμενο απο το 32bit ,τελος επιστρεφει το αθροισμα sum

Test :

Είσοδος των ακόλουθων συνδυασμών και έλεγχος εξόδων

0xCCCCCCCC - 0xBBBBBBBB

0xBBBBBBBB – 0x55555556

1. 0xCCCCCCCC – 0xBBBBBBBB

Εχουμε

Αποτελεσμα : 0x88888887

Carry out = 1

2. 0xBBBBBBBB – 0x55555556

Αποτέλεσμα : 0x11111111  
Carryout = 0

## 2 .Υλοποίηση και έλεγχος του επεξεργαστή

### 2.1 Entity MIPS

ENTITY MIPS IS port (

CLK : in std\_logic;

Rst : in std\_logic;

outMIPS : out std\_logic\_vector(31 downto 0);

);

END MIPS;



## 2.2 Εντολές

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  ENTITY InstructionMemory IS
6  port (
7      inIM : in  std_logic_vector(31 downto 0);
8      outIM : out std_logic_vector(31 downto 0)
9  );
10 END InstructionMemory;
11
12 ARCHITECTURE InstructionMemory_1 of InstructionMemory IS
13
14     type mem_type is array (natural range <>) of std_logic_vector(31 downto 0);
15     signal mem : mem_type(0 to 255) := (
16         0 => x"20000000", -- addi $0, $0, 0
17         1 => x"20040000", -- addi $4, $0, 0
18         2 => x"20030001", -- addi $3, $0, 1
19         3 => x"20050003", -- addi $5, $0, 3
20         4 => x"AC830000", -- sw $3, 0($4)
21         5 => x"20630001", -- addi $3, $3, 1
22         6 => x"20840001", -- addi $4, $4, 1
23         7 => x"20A5FFFF", -- addi $5, $5, -1
24         8 => x"14A0FFFB", -- bne $5, $0, L1 (-5)
25         others => x"00000000"
26     );
27
28     signal FullInstruction : std_logic_vector(31 downto 0);
29
30 BEGIN
31
32     process(inIM)
33         variable addr : integer;
34     begin
35         addr := to_integer(unsigned(inIM));
36
37         if (addr >= 0 and addr <= 255) then
38             FullInstruction <= mem(addr);
39         else
40             FullInstruction <= x"00000000";
41             assert false
42                 report "Instruction fetch out of bounds: PC = " & integer'image(addr)
43                 severity note;
44         end if;
45     end process;
46
47     outIM <= FullInstruction;
48
49 END InstructionMemory_1;
50
```

## 2.3 Ανάπτυξη architecture του MIPS

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  ENTITY MIPS IS
6  port (
7      CLK      : in  std_logic;
8      Rst      : in  std_logic;
9      outMIPS  : out std_logic_vector(31 downto 0);
10
11      -- Debug outputs for waveforms
12      debug_PC : out std_logic_vector(31 downto 0);
13      debug_instruction : out std_logic_vector(31 downto 0);
14      debug_reg_data1 : out std_logic_vector(31 downto 0);
15      debug_reg_data2 : out std_logic_vector(31 downto 0);
16      debug_alu_result : out std_logic_vector(31 downto 0);
17      debug_mem_data : out std_logic_vector(31 downto 0);
18      debug_write_reg : out std_logic_vector(4 downto 0);
19      debug_write_data : out std_logic_vector(31 downto 0);
20      debug_mem_addr : out std_logic_vector(31 downto 0);
21      debug_controls : out std_logic_vector(7 downto 0) -- RegWrite, ALUSrc, MemWrite, MemRead, RegDst, MemToReg, Jump, Branch
22  );
23  END MIPS;
24
25  ARCHITECTURE MIPS_1 of MIPS is
26
27      component FullAdder
28      port (
29          in1, in2 : in  std_logic_vector(31 downto 0);
30          carryin  : in  std_logic_vector(0 downto 0);
31          sum      : out std_logic_vector(31 downto 0);
32          carryout : out std_logic;
33      end component;
34
35      component ALU
36      port (
37          in1 : in std_logic_vector(31 downto 0);
38          in2 : in std_logic_vector(31 downto 0);
39          op  : in std_logic_vector(3 downto 0);
40          outALU : out std_logic_vector(31 downto 0);
41          Zero   : out std_logic;
42      end component;
43
44      component ProgramCounter
45      port (
46          inPC : in  std_logic_vector(31 downto 0);
47          outPC : out std_logic_vector(31 downto 0);
48          CLK   : in  std_logic;
49          Rst   : in  std_logic;
50      end component;
51
52      component InstructionMemory
53      port (
54          inIM : in  std_logic_vector(31 downto 0);
55          outIM : out std_logic_vector(31 downto 0);
56      end component;
57
58      component Registers
59      port (
60          CLK      : in  std_logic;
61          RegIn1   : in  std_logic_vector(4 downto 0);
62          RegIn2   : in  std_logic_vector(4 downto 0);
63          RegWriteIn : in  std_logic_vector(4 downto 0);
64          DataWriteIn : in  std_logic_vector(31 downto 0);
65          RegWrite  : in  std_logic;
66          RegOut1   : out std_logic_vector(31 downto 0);
67          RegOut2   : out std_logic_vector(31 downto 0));

```

```

68     end component;
69
70     component ALUControl
71     port (
72         ALUOp      : in  std_logic_vector(2 downto 0);
73         Funct      : in  std_logic_vector(5 downto 0);
74         ALUCont_out : out std_logic_vector(3 downto 0));
75     end component;
76
77     component OutputControl
78     port (
79         CLK        : in  std_logic;
80         OC_in      : in  std_logic_vector(5 downto 0);
81         RegWrite   : out std_logic;
82         ALUSrc     : out std_logic;
83         ALUOp      : out std_logic_vector(2 downto 0);
84         MemWrite   : out std_logic;
85         MemRead    : out std_logic;
86         RegDst     : out std_logic;
87         MemToReg   : out std_logic;
88         Jump       : out std_logic;
89         Branch     : out std_logic);
90     end component;
91
92     component Memory
93     port (
94         CLK        : in  std_logic;
95         inRAM      : in  std_logic_vector(31 downto 0);
96         WriteData  : in  std_logic_vector(31 downto 0);
97         MemWrite   : in  std_logic;
98         MemRead    : in  std_logic;
99         outRAM     : out std_logic_vector(31 downto 0);
100        reset      : in  std_logic);
101     end component;
102
103     component MUX2_5
104     port (
105         MUXIn1     : in  std_logic_vector(4 downto 0);
106         MUXIn2     : in  std_logic_vector(4 downto 0);
107         MUXOut     : out std_logic_vector(4 downto 0);
108         sel        : in  std_logic);
109     end component;
110
111     component MUX2_32
112     port (
113         MUXIn1     : in  std_logic_vector(31 downto 0);
114         MUXIn2     : in  std_logic_vector(31 downto 0);
115         MUXOut     : out std_logic_vector(31 downto 0);
116         sel        : in  std_logic);
117     end component;
118
119     component SignExtend
120     port (
121         SignExIn   : in  std_logic_vector(15 downto 0);
122         SignExOut  : out std_logic_vector(31 downto 0));
123     end component;
124
125     -- Signals
126     signal RegWrite, ALUSrc, MemWrite, MemRead, RegDst, MemToReg, Jump, Zero, Branch, BranchTaken : std_logic;
127     signal PC_FA_IM, FA_PC_OUT, OUT_IM, ONE, outALU : std_logic_vector(31 downto 0);
128     signal ALUOp : std_logic_vector(2 downto 0);
129     signal RegOut1, RegOut2, DataWriteIn, MUXaluOut, SignExOut, outRAM, ShiftJump2MuxJump, MuxJump2PC, MuxBranch2MuxJump, ALUbranchOut,
130     signal ALUControl_out : std_logic_vector(3 downto 0);
131     signal MUXregOut : std_logic_vector(4 downto 0);

```

```

132
133 BEGIN
134
135 -- PC increment and branch calc
136 ONE <= std_logic_vector(to_unsigned(1,32));
137 PC_plus_1 <= std_logic_vector(unsigned(PC_FA_IM) + unsigned(ONE));
138
139
140 PC_branch_target <= std_logic_vector(signed(PC_plus_1) + signed(SignExOut));
141
142 -- Program Counter
143 PC1: ProgramCounter
144   port map(
145     inPC => MuxJump2PC,
146     outPC => PC_FA_IM,
147     CLK  => CLK,
148     Rst  => Rst);
149
150 -- Instruction Memory
151 IM1: InstructionMemory
152   port map(
153     inIM => PC_FA_IM,
154     outIM => OUT_IM);
155
156 -- Register File
157 REG1: Registers
158   port map(
159     CLK      => CLK,
160     RegIn1   => OUT_IM(25 downto 21),
161     RegIn2   => OUT_IM(20 downto 16),
162     RegWriteIn => MUXregOut,
163     DataWriteIn => DataWriteIn,
164     RegWrite  => RegWrite,
165     RegOut1   => RegOut1,
166     RegOut2   => RegOut2);
167
168 -- Main Control Unit
169 OC1: OutputControl
170   port map(
171     CLK      => CLK,
172     OC_in    => OUT_IM(31 downto 26),
173     RegWrite => RegWrite,
174     ALUSrc  => ALUSrc,
175     ALUOp   => ALUOp,
176     MemWrite => MemWrite,
177     MemRead  => MemRead,
178     RegDst   => RegDst,
179     MemToReg => MemToReg,
180     Jump     => Jump,
181     Branch   => Branch);
182
183 -- ALU Control Unit
184 ALUC_1: ALUControl
185   port map(
186     ALUOp      => ALUOp,
187     Funct      => OUT_IM(5 downto 0),
188     ALUCont_out => ALUControl_out);
189
190 -- ALU
191 ALU1: ALU
192   port map(
193     in1  => RegOut1,
194     in2  => MUXaluOut,
195     op   => ALUControl_out,

```

```

196         outALU => outALU,
197         Zero   => Zero);
198
199 -- Data Memory
200 RAM1: Memory
201 port map(
202     CLK       => CLK,
203     inRAM     => outALU,
204     WriteData => RegOut2,
205     MemWrite  => MemWrite,
206     MemRead   => MemRead,
207     outRAM    => outRAM,
208     reset     => Rst);
209
210 -- MUXes
211 MUXreg: MUX2_5
212 port map(
213     MUXin1 => OUT_IM(20 downto 16),
214     MUXin2 => OUT_IM(15 downto 11),
215     MUXout => MUXregOut,
216     sel    => RegDst);
217
218 MUXaluIn: MUX2_32
219 port map(
220     MUXin1 => RegOut2,
221     MUXin2 => SignExOut,
222     MUXout => MUXaluOut,
223     sel    => ALUSrc);
224
225 MUXram: MUX2_32
226 port map(
227     MUXin1 => outALU,
228     MUXin2 => outRAM,
229     MUXout => DataWriteIn,
230     sel    => MemToReg);
231
232 ShiftJump2MuxJump <= PC_plus_1(31 downto 28) & OUT_IM(25 downto 0) & "00";
233
234 MUXjump: MUX2_32
235 port map(
236     MUXin1 => MuxBranch2MuxJump,
237     MUXin2 => ShiftJump2MuxJump,
238     MUXout => MuxJump2PC,
239     sel    => Jump);
240
241 -- Complete branch logic for both beq and bne
242 -- beq (000100): branch if equal (Zero = '1')
243 -- bne (000101): branch if not equal (Zero = '0')
244 BranchTaken <= Branch and Zero when OUT_IM(31 downto 26) = "000100" else -- beq
245               Branch and (not Zero) when OUT_IM(31 downto 26) = "000101" else -- bne
246               '0';
247
248 MUXbranch: MUX2_32
249 port map(
250     MUXin1 => PC_plus_1,
251     MUXin2 => PC_branch_target,
252     MUXout => MuxBranch2MuxJump,
253     sel    => BranchTaken);
254
255 SignEx1: SignExtend
256 port map(
257     SignExIn  => OUT_IM(15 downto 0),
258     SignExOut => SignExOut);
259
260 -- Debug output connections
261 debug_PC <= PC_FA_IM;
262 debug_instruction <= OUT_IM;
263 debug_reg_data1 <= RegOut1;
264 debug_reg_data2 <= RegOut2;
265 debug_alu_result <= outALU;
266 debug_mem_data <= outRAM;
267 debug_write_reg <= MUXregOut;
268 debug_write_data <= DataWriteIn;
269 debug_mem_addr <= outALU when (MemRead = '1' or MemWrite = '1') else (others => '0');
270 debug_controls <= RegWrite & ALUSrc & MemWrite & MemRead & RegDst & MemToReg & Jump & Branch;
271
272 outMIPS <= outALU;
273
274 END MIPS_1;

```

## Σχολια - Παρατηρήσεις:

Συνδέσαμε όλες τις επιμέρους μονάδες που είχαμε φτιάξει προηγουμένως για τον επεξεργαστή mips .Εχουμε : program counter που κρατά την διεύθυνση μνήμης . Να τονίσω ότι αυξάνεται στον ίδιο τον mips με pc+1 . Εχουμε, ένα instruction memory που έχουμε βάλει τις εντολές που

θελουμε να τρεξει το mips . Επιπλεον χωριζει το opcode , rs,rt,rd ,immediate και το output control παραγει τα καταλληλα σήηματα για regwrite ,alusrc,aluop etc. Οι registers διαβαζουν τα περιεχόμενα του rs ,rt . Αν alusrc = 0 τότε χρησιμοποιει τιμή απο δευτερο καταχωρητη , αν alusrc =1 τότε χρησιμοποιει signextended immediate , η alu εκτελει τη πραξη και δινει αποτελεσμα ,δηλαδη outalu και σημα zero . Επίσης εχουμε memory access με χρηση εντολών οπως lw ,sw και τα σήηματα memwrite οπου διαβαζει απο outalu ,memread γραφει στον regout2 . Εχουμε και memtoreg που γραφει απο μνημη σε καταχωρητη και υπολογισμο pc .Αν jumb=1 τότε πηγανει στο jumb address , αν branch =1 και zero =1 τότε κανει branch ,άλλιως κανει pc+1.

Εχω βαλει στο entity debugs διοτι επερνα καποια λαθη οπως iteration erros , αρνητικο pc , branch faults και ηθελα να δω ακριβως τι γινεται στον επεξεργαστη οποτε θα δουμε μια πληρης εικονα του επεξεργαστη αργοτερα

## 2.4 Προσομοίωση - Έλεγχος λειτουργιών

### 2.4.1 Ρυθμιση ρολογιού

Θελουμε συχνότητα 200Mhz, Αρα  $T=1/f \Rightarrow T = 1/200 * 10^6 = 5 \text{ ns}$

Ολοκληρη η περιοδος πρεπει να ειναι 5 ns ,

Αρα οταν ειναι high ο παλμος πρεπει να διαρκεσει 2.5ns και οταν ειναι low πάλι 2.5ns ,ετσι ενας πληρης κύκλος ειναι 5 ns.

```
clk_process: process
```

```
begin
```

```
while true loop
```

```
    CLK <= '1';
```

```
    wait for 2.5 ns;
```

```
    CLK <= '0';
```

```
    wait for 2.5 ns;
```

```
end loop;
```

```
end process;
```

### 2.4.2 Reset

```
rst_process: process
begin
    Rst <= '1';
    wait for 12.5 ns;
    Rst <= '0';
    wait;
end process;
```

## 2.4.3 Προσομοίωση

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  ENTITY TestBench is
6  END TestBench;
7
8  ARCHITECTURE TestBench_MIPS of TestBench is
9
10 component MIPS
11     port (
12         CLK : in std_logic;
13         Rst : in std_logic;
14         outMIPS : out std_logic_vector(31 downto 0);
15         -- Debug outputs
16         debug_PC : out std_logic_vector(31 downto 0);
17         debug_instruction : out std_logic_vector(31 downto 0);
18         debug_reg_data1 : out std_logic_vector(31 downto 0);
19         debug_reg_data2 : out std_logic_vector(31 downto 0);
20         debug_alu_result : out std_logic_vector(31 downto 0);
21         debug_mem_data : out std_logic_vector(31 downto 0);
22         debug_write_reg : out std_logic_vector(4 downto 0);
23         debug_write_data : out std_logic_vector(31 downto 0);
24         debug_mem_addr : out std_logic_vector(31 downto 0);
25         debug_controls : out std_logic_vector(7 downto 0)
26     );
27 end component;
28
29 -- signals
30 signal CLK : std_logic := '0';
31 signal Rst : std_logic := '1';
32 signal outMIPS : std_logic_vector(31 downto 0);
33
34 -- Debug signals waveform viewing
35 signal debug_PC : std_logic_vector(31 downto 0);
36 signal debug_instruction : std_logic_vector(31 downto 0);
37 signal debug_reg_data1 : std_logic_vector(31 downto 0);
38 signal debug_reg_data2 : std_logic_vector(31 downto 0);
39 signal debug_alu_result : std_logic_vector(31 downto 0);
40 signal debug_mem_data : std_logic_vector(31 downto 0);
41 signal debug_write_reg : std_logic_vector(4 downto 0);
42 signal debug_write_data : std_logic_vector(31 downto 0);
43 signal debug_mem_addr : std_logic_vector(31 downto 0);
44 signal debug_controls : std_logic_vector(7 downto 0);
45
46 -- control signals
47 signal RegWrite : std_logic;
48 signal ALUSrc : std_logic;
49 signal MemWrite : std_logic;
50 signal MemRead : std_logic;
51 signal RegDst : std_logic;
52 signal MemToReg : std_logic;
53 signal Jump : std_logic;
54 signal Branch : std_logic;
55
56 -- Instruction decoding signals
57 signal opcode : std_logic_vector(5 downto 0);
58 signal rs : std_logic_vector(4 downto 0);
59 signal rt : std_logic_vector(4 downto 0);
60 signal rd : std_logic_vector(4 downto 0);
61 signal immediate : std_logic_vector(15 downto 0);
62 signal jump_addr : std_logic_vector(25 downto 0);
63
64
65 signal reg_write_occurred : std_logic := '0';
66 signal prev_write_reg : std_logic_vector(4 downto 0) := (others => '0');
67 signal prev_write_data : std_logic_vector(31 downto 0) := (others => '0');
68
69
70 signal mem_write_occurred : std_logic := '0';
71 signal mem_read_occurred : std_logic := '0';
```

Ctrl+A	Select All
Ctrl+G	Goto
Ctrl+H	Replace
Ctrl+U	Delete Line
Ctrl+W	Add Selection T
	View All Short
Ctrl+F	Find in Files



```


72 signal prev_mem_addr : std_logic_vector(31 downto 0) := (others => '0');
73 signal prev_mem_data : std_logic_vector(31 downto 0) := (others => '0');
74
75 BEGIN
76
77 UUT: MIPS
78   port map (
79     CLK => CLK,
80     Rst => Rst,
81     outMIPS => outMIPS,
82     debug_PC => debug_PC,
83     debug_instruction => debug_instruction,
84     debug_reg_data1 => debug_reg_data1,
85     debug_reg_data2 => debug_reg_data2,
86     debug_alu_result => debug_alu_result,
87     debug_mem_data => debug_mem_data,
88     debug_write_reg => debug_write_reg,
89     debug_write_data => debug_write_data,
90     debug_mem_addr => debug_mem_addr,
91     debug_controls => debug_controls
92   );
93
94
95 RegWrite <= debug_controls(7);
96 ALUSrc <= debug_controls(6);
97 MemWrite <= debug_controls(5);
98 MemRead <= debug_controls(4);
99 RegDst <= debug_controls(3);
100 MemToReg <= debug_controls(2);
101 Jump <= debug_controls(1);
102 Branch <= debug_controls(0);
103
104
105 opcode <= debug_instruction(31 downto 26);
106 rs <= debug_instruction(25 downto 21);
107 rt <= debug_instruction(20 downto 16);
108 rd <= debug_instruction(15 downto 11);
109 immediate <= debug_instruction(15 downto 0);
110 jump_addr <= debug_instruction(25 downto 0);
111
112 -- Clock generation: 200 MHz, period = 5 ns
113 clk_process: process
114 begin
115   while true loop
116     CLK <= '1';
117     wait for 2.5 ns;
118     CLK <= '0';
119     wait for 2.5 ns;
120   end loop;
121 end process;
122
123 -- Reset
124 rst_process: process
125 begin
126   Rst <= '1';
127   wait for 12.5 ns;
128   Rst <= '0';
129   wait;
130 end process;
131
132 -- Process
133 reg_monitor: process(CLK)
134 begin
135   if rising_edge(CLK) then
136     if RegWrite = '1' and Rst = '0' then
137       reg_write_occurred <= '1';
138       prev_write_reg <= debug_write_reg;
139       prev_write_data <= debug_write_data;
140
141       else
142         reg_write_occurred <= '0';
143       end if;
144     end if;
145   end process;
146
147 -- Process
148 mem_monitor: process(CLK)
149 begin
150   if rising_edge(CLK) then
151     if Rst = '0' then
152       if MemWrite = '1' then
153         mem_write_occurred <= '1';
154         prev_mem_addr <= debug_mem_addr;
155         prev_mem_data <= debug_reg_data2;
156       else
157         mem_write_occurred <= '0';
158       end if;
159
160       if MemRead = '1' then
161         mem_read_occurred <= '1';
162         prev_mem_addr <= debug_mem_addr;
163         prev_mem_data <= debug_mem_data;
164       else
165         mem_read_occurred <= '0';
166       end if;
167     else
168       mem_write_occurred <= '0';
169       mem_read_occurred <= '0';
170     end if;
171   end process;
172
173 END TestBench_MIPS;

```


Σχολια - Παρατηρήσεις

Εχουμε 200Mhz συχνοτητα ,κανω monitor τους register να βλεπω ακριβως τι γινεται οπως και memory monitor ,κανω signal assignments RegWrite <= debug\_controls(7) και αναλυση εντολω , opcode <= debug\_instruction(31 downto 26); κτλπ


## 2.3.4 ΑΠΟΤΕΛΕΣΜΑΤΑ :

 

15ns – 30ns

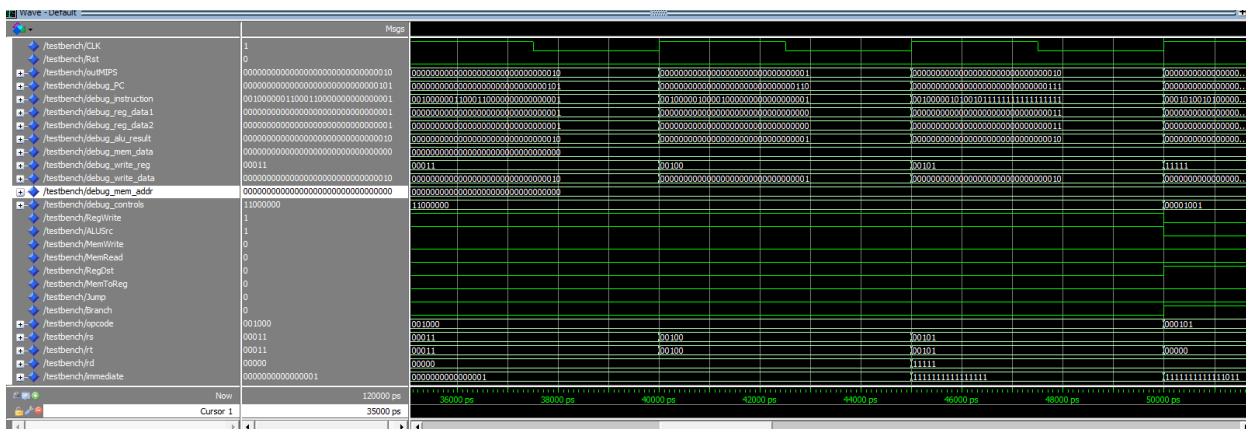

35-50ns

 

55- 64ns branch γίνεται 1 . Pc απο 8 γίνεται 4

Ας δουμε τι γίνεται αναλυτικά:

15 ns ,εχουμε pc = 0 , και η πρωτη μας εντολη ειναι η addi \$0, \$0, 0 . Και απλα κανει τον \$0 , μηδεν , εχουμε reg used = 0 ,immediate = 0, alu result = 0 και control signals :

Regwrite = 1

Alusrc = 1

Regdst=0

Memtoreg=0

Memwrite = 0

Memread = 0

Jumb = 0

Branch = 0

20ns 15 ns ,εχουμε pc = 1 , και η δευτερη μας εντολη ειναι η addi \$4, \$0, 0 . Και απλα κανει τον \$4 , μηδεν regwrite \$0,0 ignored.

Επειτα 25ns addi \$3, \$0, 1

Βαζει στον καταχωρητη \$3 το 1 και εχουμε aluresult =1

30ns pc =3 , intruction = addi \$5, \$0, 3

Alu result = 3

Στα 35 ns εχουμε sw \$3, 0(\$4), κανει store \$3 δηλαδη το 1 στο mem \$4, alu = 0 και signals RegWrite=0, MemWrite=1, ALUSrc=1


Στα 40ns pc = 5 , intructions = addi \$3, \$3, 1 , αρα γίνεται 2 ο καταχωρητης 3, aluresult = 2

Στα 45 ns pc = 6 , instructions = addi \$4, \$4, 1, κανει το \$4 ,1

Στα 50 ns pc = 7 , instructions = addi \$5, \$5, -1, κανει αφαιρεση τον\$5 απο 3 σε 2, Alu result = 2

Στα 55ns pc = 8 ,instructions = bne \$5, \$0, -5, το \$5 δεν ειναι ισο με \$0 αρα παει πισω στο branch, pc = 4,control signals : Branch=1, RegWrite=0, MemWrite=0

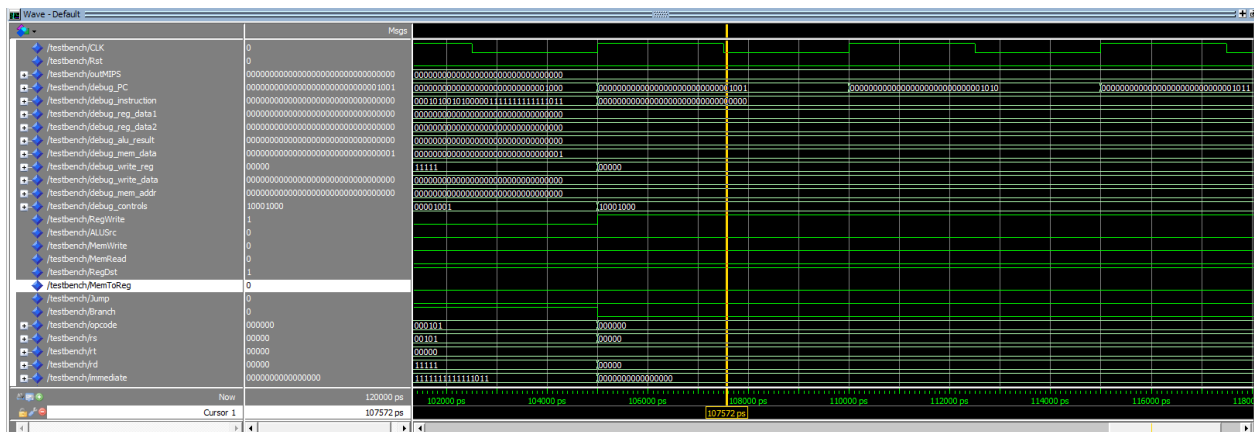Αρα επαναλαμβανει αυτο αλλες 2 φορες μεχρι οτου το \$5 να ειναι = με \$0 δηλαδη με 0 .



Εδω βγαινει απο Loop. Η προσωμίωση ετρεξε περιπου για 20-22 εφοσον βγει απο τη λουπα